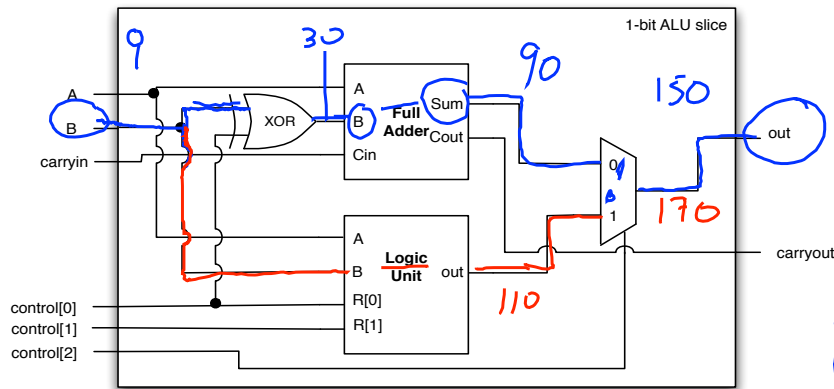


Computing components from ALU1



What is the worst case propagation delay from B to out?
(consider both arithmetic and logic operations)

- A: 120ps
- B: 150ps
- C: 160ps
- D: 170ps
- E: 190ps

XOR gate	In	Out	Delay
	A, B	out	30ps

Full Adder	In	Out	Delay
	A, B	Sum	60ps
	Cin	Sum	30ps
	A, B	Cout	90ps
	Cin	Cout	60ps

Logic Unit	In	Out	Delay
	A, B	out	110ps
	R	out	10ps

2-to-1 Multiplexor	In	Out	Delay
	A, B	out	60ps
	R	out	80ps


Sequential Logic & Finite State Machines

Today's lecture

- **Sequential Logic**
- **Synchronous Design**
- **Goal: Build a sequential circuit from a state diagram**
 - Step 0: Problem specification
 - Step 1: Build the state diagram
 - Step 2: Build the state table
 - Step 3: Build the sequential circuit using D flip-flops
- **Timing diagram**
- **Another example: Sequence recognizer**


Sequential Logic

 - A circuit whose output depends not only on the present value of its input signals but on the sequence of past inputs
 - The input history.
- That is, **sequential logic** has state (memory) while **combinational logic** does not.




Synchronous Design

 - *The easiest (and most common) way to build computers*
- All state elements get updated at the same time
 - Using a clock signal
- Clock signal
 - A square wave with a constant period




- We always update state at the same point in wave
 - E.g., the rising edge

Synchronous Design, cont.

 


 
- Alternate between computation and updating state.




The state element that we really want...

■ The D flip flop

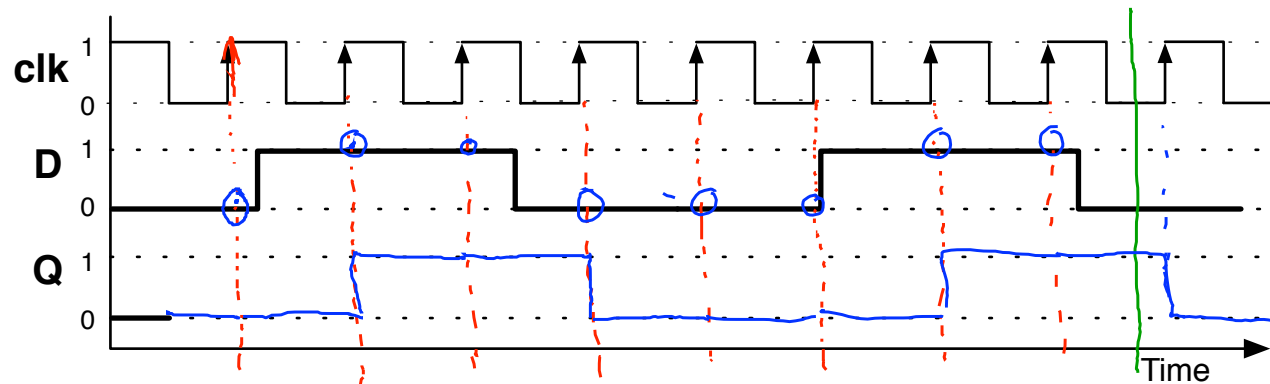 - Holds 1 bit of state
 - Output as Q.
- Inputs
 - Copies D input into state on rising edge of clock.



Finite State Machine (Moore machine)

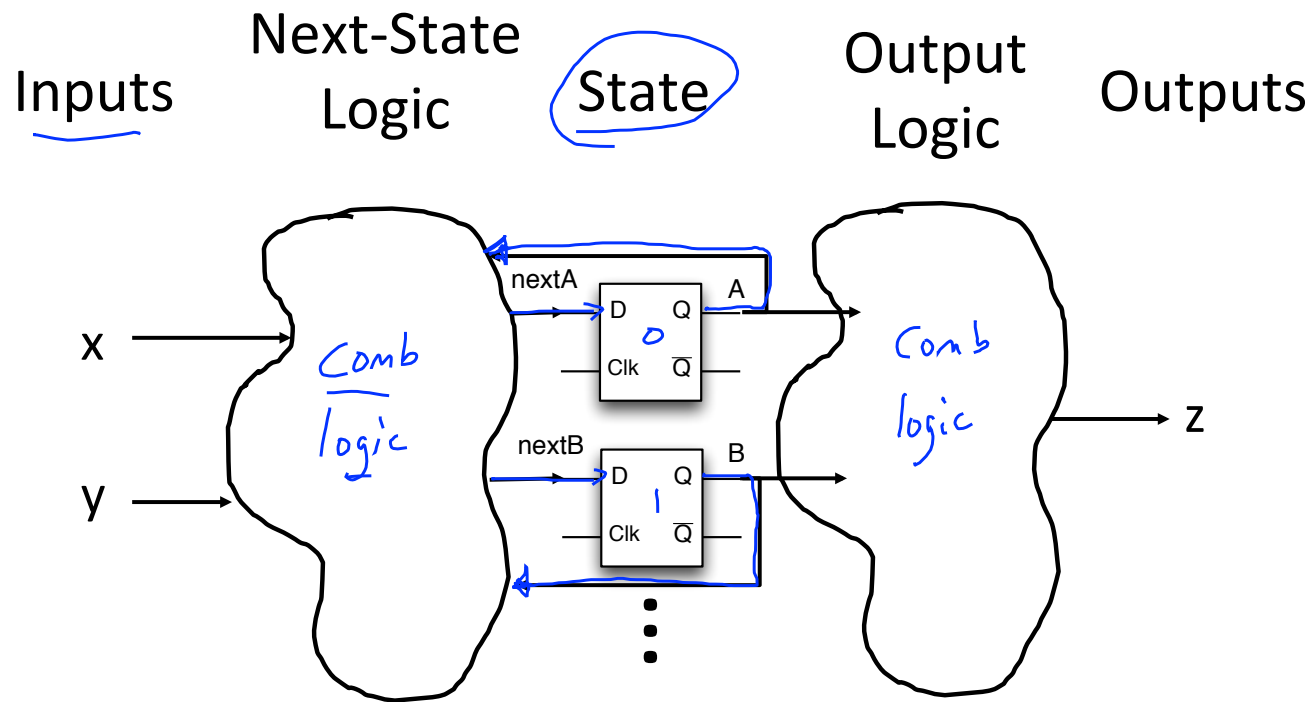

Step 0: Problem Specification

- We have a candy machine that dispenses candies that cost 15-cents
 - Accepts
 - nickels (5-cents)
 - dimes (10-cents)
 - Dispenses a candy if the balance is ≥ 15 -cents
 - When the customer overpays
 - the machine does not return change, but
 - keeps the balance for future transactions



Step 1: Build the State Diagram

- Inputs

<u>d n</u>	
1 0	dime (10)
0 1	nickel (5)
0 0	nothing (0)

- Outputs

<u>c</u>	
0	no candy for you.
1	dispense candy

- State identification

balance of 0 cents
 " " 5 "
 " " 10 cents
 " " 15 cents
 " " 20 cents

3 states.

Step 1: Build the State Diagram

Outputs: candy or candy'

Got-0,
candy'

Got-5,
candy


Got-10
candy'

Got-15
candy

Got-20
candy

- a) candy
- b) candy'

Step 1: Build the State Diagram

 

Inputs: $d'n'$, $d'n$, dn'
 \emptyset 5 10

Step 1: Build the State Diagram iClicker®

What are the transitions for state Got-15?


A: d'n': Got0; d'n: Got20; dn': Got20

B: d'n': Got0; d'n: Got0; dn': Got0


C: d'n': Got0; d'n: Got5; dn': Got10

D: d'n': Got15; d'n: Got5; dn': Got10


Inputs: d'n', d'n, dn'

 

Final State Diagram

 

Step 2: Build a State Table

 


Current State	Output candy
A	0
B	0
C	0
D	1
E	1

15
20

$$\text{candy} = D + E;$$


In a 'Moore machine', the outputs are a function only of the current state.

Step 2: Build a Next-State Table

 

Current State	Input	Next State					
<u>A</u>	<u>d'n'</u>	<u>A</u>					
<u>A</u>	<u>d'n</u>	<u>B</u>					
<u>A</u>	<u>dn'</u>	<u>C</u>	A	B	C	D	E
<u>B</u>	<u>d'n'</u>	<u>B</u>	A	B	B	B	C
<u>B</u>	<u>d'n</u>	<u>C</u>	B	C	C	D	D
<u>B</u>	<u>dn'</u>	<u>D</u>	C	D	E	A	E
C	d'n'						
C	d'n						
C	dn'						
D	d'n'						
D	d'n						
D	dn'						
E	d'n'						
E	d'n						
E	dn'						


Step 2: Build a Next-State Table

 

Why do we need sequential logic to build this circuit?

Current State	Input	Next State
A	$d'n'$	A
A	$d'n$	B
A	dn'	C
B	$d'n'$	B
B	$d'n$	C
B	dn'	D
C	$d'n'$	C
C	$d'n$	D
C	dn'	E
D	$d'n'$	A
D	$d'n$	B
D	dn'	C
E	$d'n'$	B
E	$d'n$	C
E	dn'	D

Step 3: Build Sequential Circuit

 

Step 3: Build Sequential Circuit (State)

Current State	Input	Next State
A	d'n'	A
A	d'n	B
A	dn'	C
B	d'n'	B
B	d'n	C
B	dn'	D
C	d'n'	C
C	d'n	D
C	dn'	E
D	d'n'	A
D	d'n	B
D	dn'	C
E	d'n'	B
E	d'n	C
E	dn'	D

State Encoding:

5 states: How many bits?

- a) 2
- b) 3 ✓
- c) 4
- d) 5
- e) 6

5 flip flops

~~minimum~~

$$2^2 = 4$$

$$2^3 = 8$$

Step 3: Build Sequential Circuit (State)

Current State	Input	Next State
<u>A</u>	d'n'	<u>A</u>
<u>A</u>	d'n	B
<u>A</u>	dn'	C
B	d'n'	B
B	d'n	C
B	dn'	D
C	d'n'	C
C	d'n	D
C	dn'	E
<u>D</u>	<u>d'n'</u>	<u>A</u>
D	d'n	B
D	dn'	C
E	d'n'	B
E	d'n	C
E	dn'	D

One hot encoding

ABCDE

State A = 10000


State B = 01000

State C = 00100


State D = 00010

State E = 00001

$$\text{nextA} = A d'n' + D d'n'$$

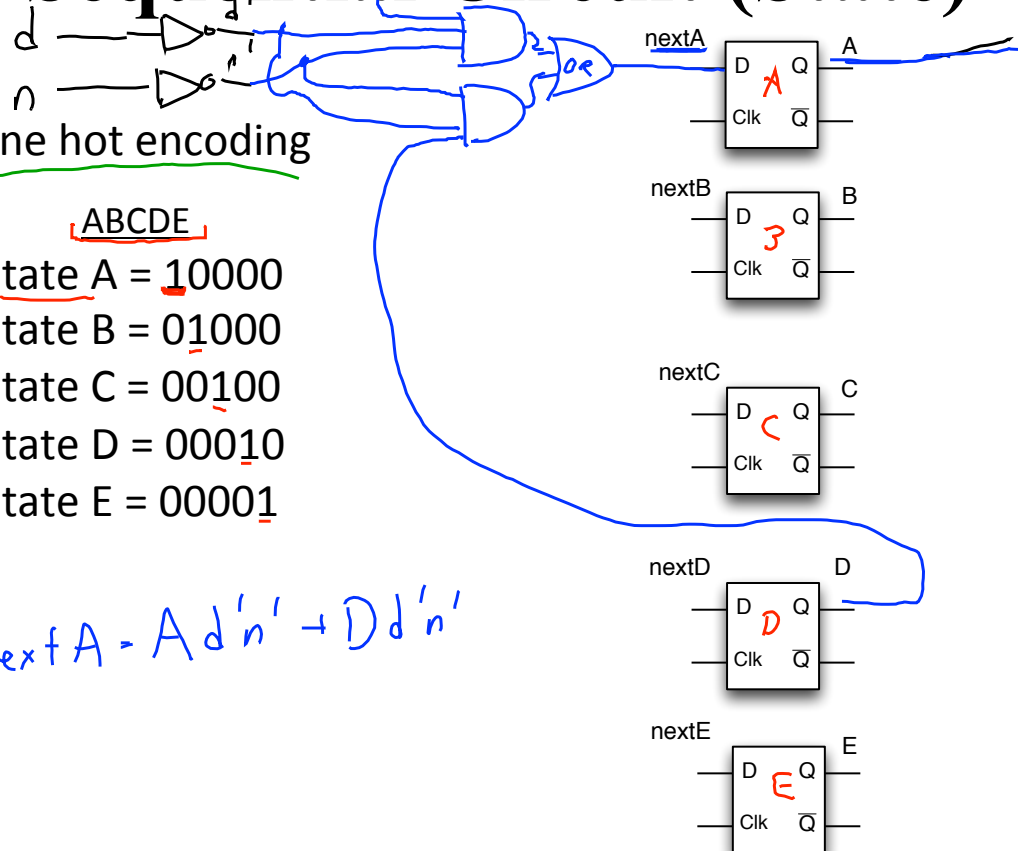

Step 3: Build Sequential Circuit

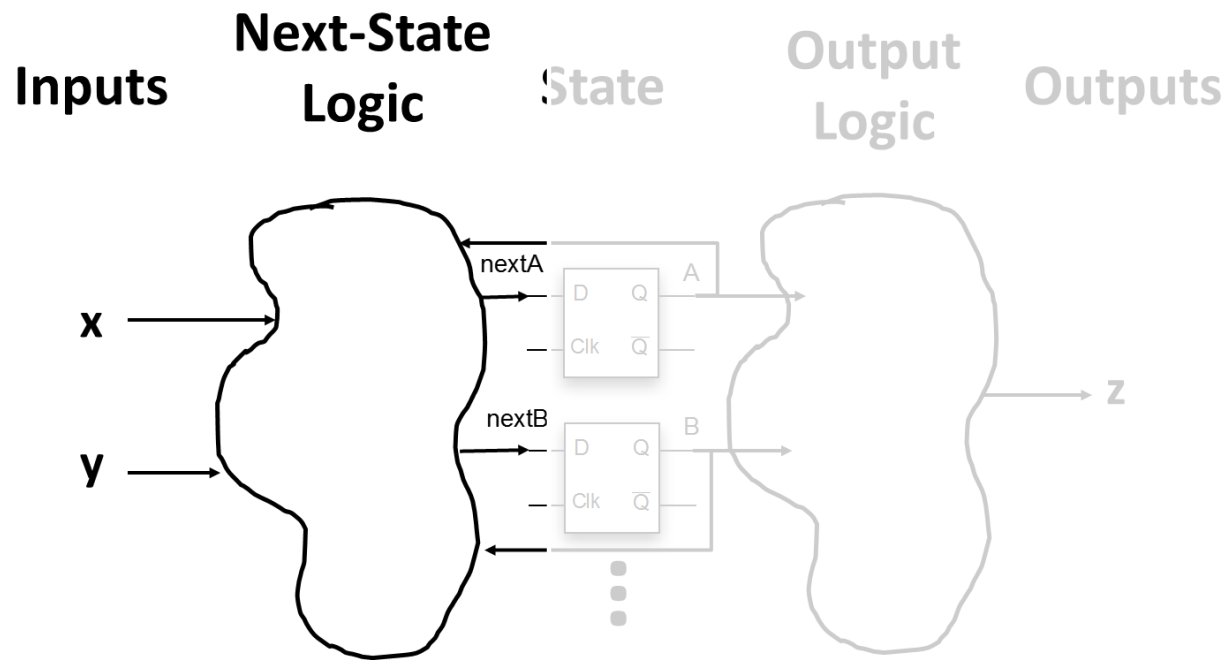

Step 3: Build Sequential Circuit (Next-State Logic)

Current State	Input	Next State
A	d'n'	A
A	d'n	B
A	dn'	C
B	d'n'	B
B	d'n	C
<u>B</u>	<u>dn'</u>	<u>D</u>
C	d'n'	C
<u>C</u>	<u>d'n</u>	<u>D</u>
C	dn'	E
D	d'n'	A
D	d'n	B
D	dn'	C
E	d'n'	B
E	d'n	C
<u>E</u>	<u>dn'</u>	<u>D</u>

next D?






$$A: \text{nextD} = Ad'n' + Dd'n'$$

$$B: \text{nextD} = Ad'n + Bd'n' + Dd'n$$


$$C: \text{nextD} = Bdn' + Cd'n + Edn'$$

$$D: \text{nextD} = Ad'n' + Bd'n + Cdn'$$

$$E: \text{nextD} = 1$$

     

Step 3: Build Sequential Circuit

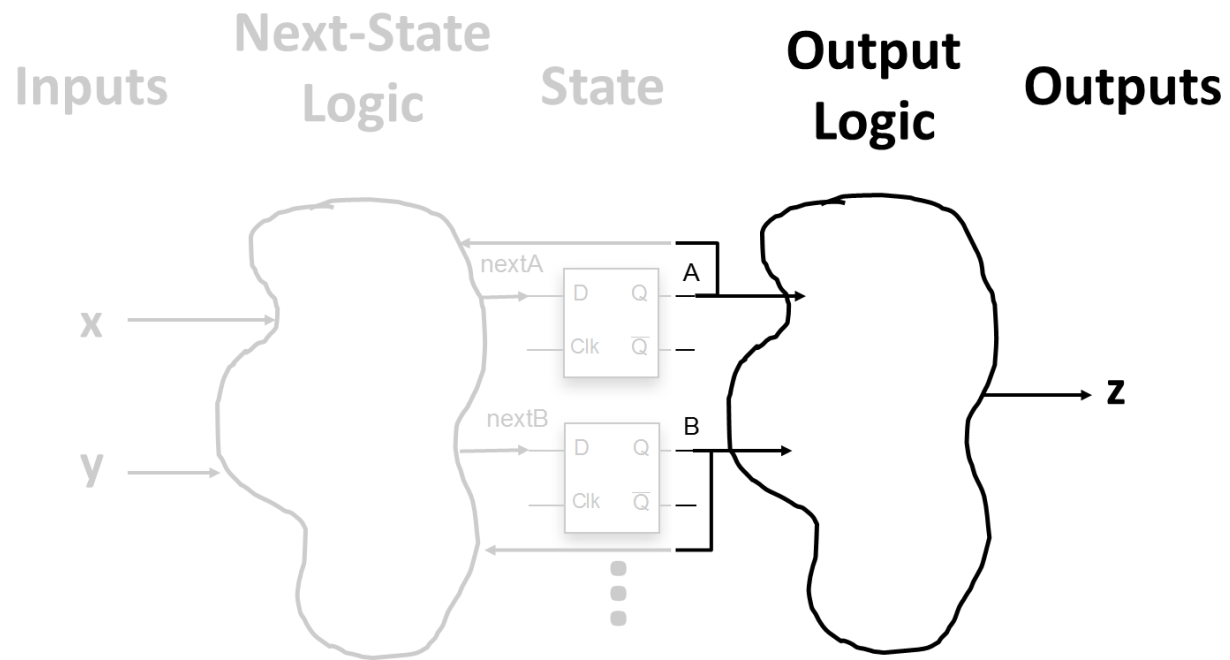

Step 3: Build Sequential Circuit (output logic)

Current State	Input	Next State	Output
A	d'n'	A	0
A	d'n	B	0
A	dn'	C	0
B	d'n'	B	0
B	d'n	C	0
B	dn'	D	0
C	d'n'	C	0
C	d'n	D	0
C	dn'	E	0
D	d'n'	A	1
D	d'n	B	1
D	dn'	C	1
E	d'n'	B	1
E	d'n	C	1
E	dn'	D	1

$$\text{nextA} = Ad'n' + Dd'n'$$

$$\text{nextB} = Ad'n + Bd'n' + Dd'n + Edn'$$

$$\text{nextC} = And' + Bd'n + Cd'n' + Ddn' + Ed'n$$

$$\text{nextD} = Bdn' + Cd'n + Edn'$$


$$\text{nextE} = Cdn'$$

$$\text{Output: Candy} = \underline{D} + \underline{E}$$

Step 3: Build Sequential Circuit (output logic)

$$\begin{aligned} \text{nextA} &= Ad'n' + Dd'n' \\ \text{nextB} &= Ad'n + Bd'n' + Dd'n + Edn' \\ \text{nextC} &= And' + Bd'n + Cd'n' + Ddn' + Ed'n \\ \text{nextD} &= Bdn' + Cd'n + Edn' \\ \text{nextE} &= Cdn' \end{aligned}$$


Output: $c = D + E$

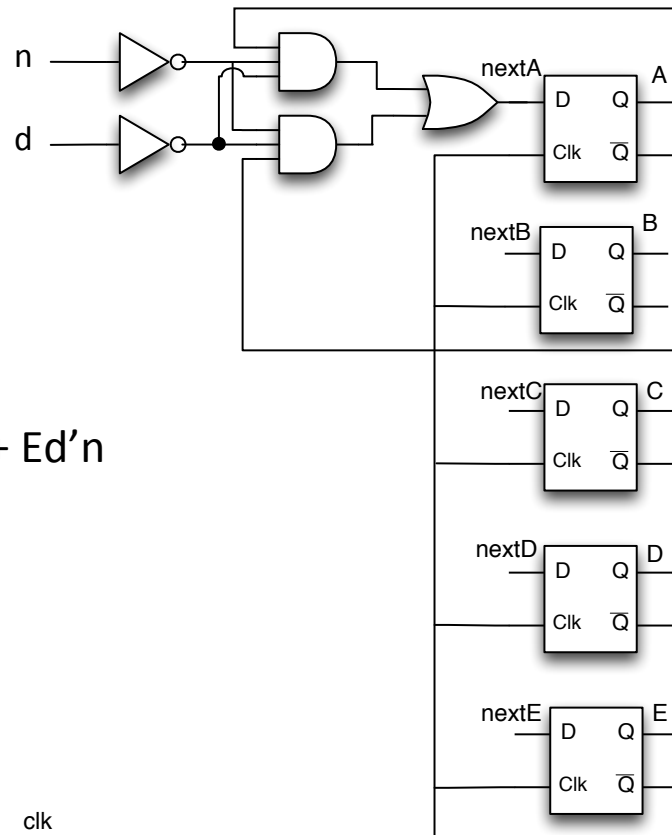


Step 3: Build Sequential Circuit (“finished”)

$$\begin{aligned} \text{nextA} &= Ad'n' + Dd'n' \\ \text{nextB} &= Ad'n + Bd'n' + Dd'n + Edn' \\ \text{nextC} &= And' + Bd'n + Cd'n' + Ddn' + Ed'n \\ \text{nextD} &= Bdn' + Cd'n + Edn' \\ \text{nextE} &= Cdn' \end{aligned}$$


$$\text{Output} = \text{Candy} = D + E$$

 

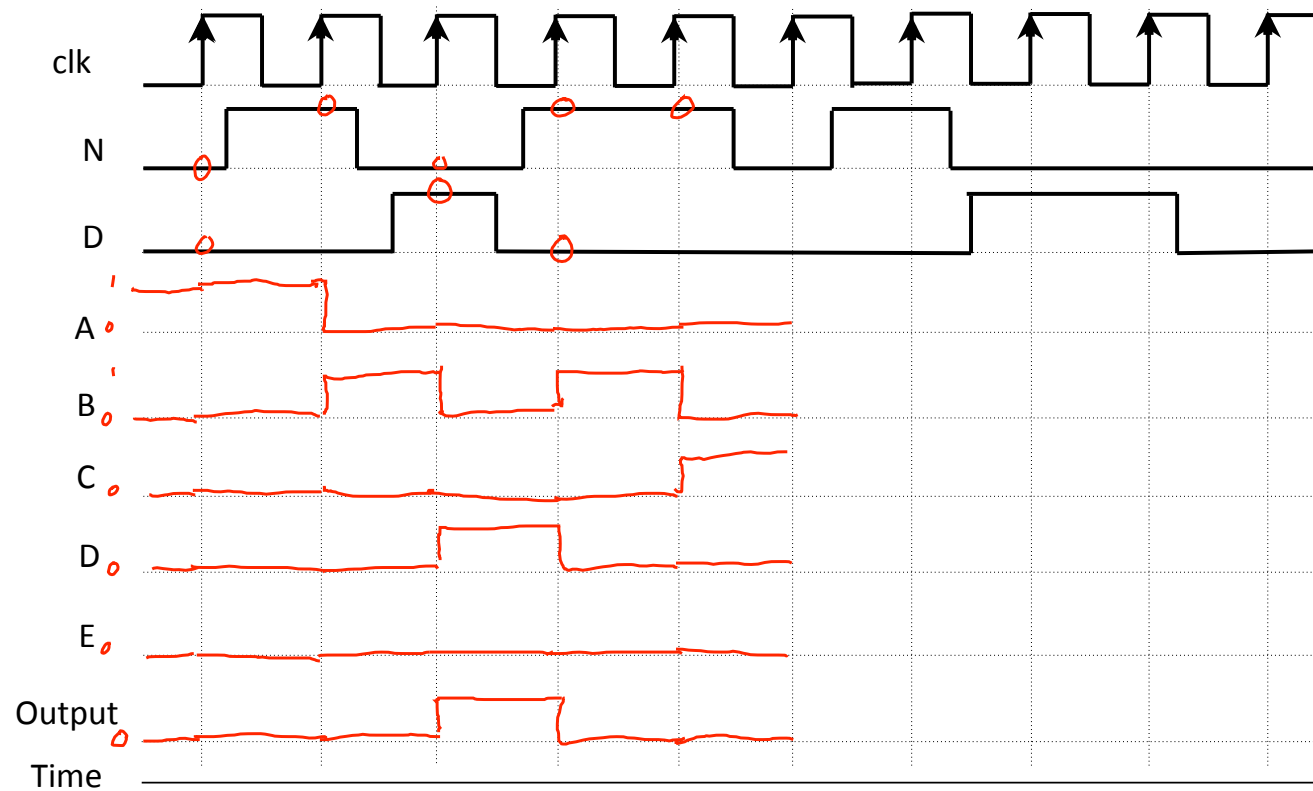Timing Diagram (update state on clock edges)




Timing Diagram

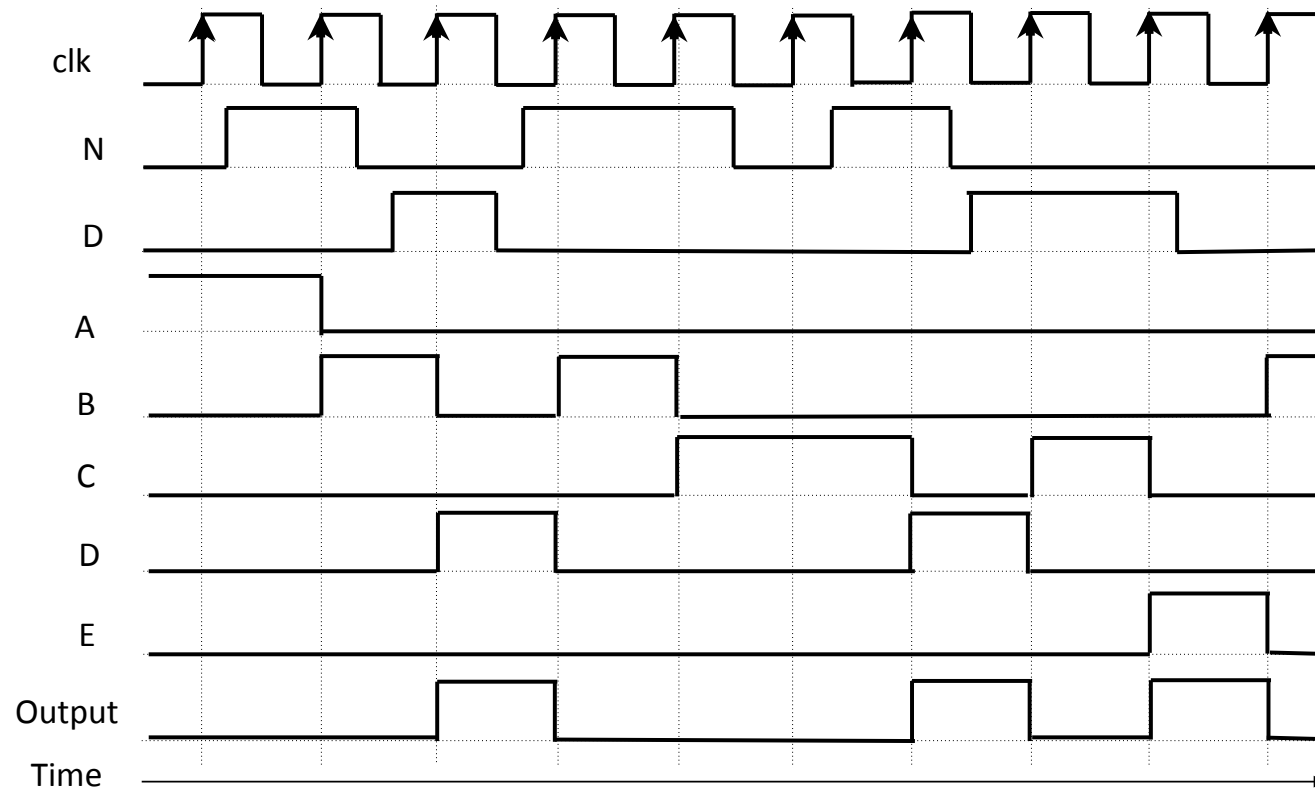

Another example: Sequence recognizer

 - A **sequence recognizer** is a special kind of sequential circuit that looks for a special bit pattern in some input.
- The recognizer circuit has one input, X.
- There is one output, Z, which is 1 when the desired pattern is found.



- Our example will detect the bit pattern “1001”:


Inputs: 1 1 1001 10 1001 001 10 ...

Outputs: 000000 1 000000 1 00 1 0 ...

Here, one input and one output bit appear every clock cycle.


- This requires a sequential circuit because the circuit has to “remember” the inputs from previous clock cycles, in order to determine whether or not a match was found.

State diagram

 

State	Meaning
A	None of the <u>desired pattern</u> (1001) has been input yet.
B	We've already seen the first bit (1) of the desired pattern.
C	We've already seen the first two bits (10) of the desired pattern.
D	We've already seen the first three bits (100) of the desired pattern.
E	We've seen the pattern (1001)

State diagram

 


State	Meaning
A	None of the desired pattern (1001) has been input yet.
B	We've already seen the first bit (1) of the desired pattern.
C	We've already seen the first two bits (10) of the desired pattern.
D	We've already seen the first three bits (100) of the desired pattern.
E	We've seen the pattern (1001)

State diagram



 - We need *two* outgoing arrows for each node, to account for the possibilities of $X=0$ and $X=1$.



Inputs: 1 1 1 0 0 1 1 0 1 0 0 1 0 0 1 1 0 ...
Outputs: 0 0 0 0 0 0 1 0 0 0 0 0 1 0 0 1 0 ...

Transitions for E:

A: $x=0 \rightarrow A$; $x=1 \rightarrow B$


B: $x=0 \rightarrow C$; $x=1 \rightarrow B$

C: $x=0 \rightarrow B$; $x=1 \rightarrow A$

D: $x=0 \rightarrow D$; $x=1 \rightarrow B$


State diagram

 - We need *two* outgoing arrows for each node, to account for the possibilities of $X=0$ and $X=1$.




State diagram

- Need to determine the output

 


State Table

 

Current State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	E	1
E	0	C	0
E	1	B	0

State Table

 

Current State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	E	1
E	0	C	0
E	1	B	0

$$A_{next} = Ax' + Dx'$$

$$B_{next} = Ax + Bx + Cx + Ex$$

$$C_{next} = Bx' + Ex'$$

$$D_{next} = Cx'$$

$$E_{next} = Dx$$

$$\text{Output} = E$$