

Exam 1 is live

## Registers and Register Files


PICK UP HANDOUT.

# State – the central concept of computing

Computer can do 2 things

1) Store state (How do we actually store bits?)

2) Manipulate state


 


# Today's lecture

- More D Flip flops
  - Asynchronous reset
  - Enable
- Random Access Memory (RAM)
  - Addressable storage
- Register Files
  - Registers
  - Decoders
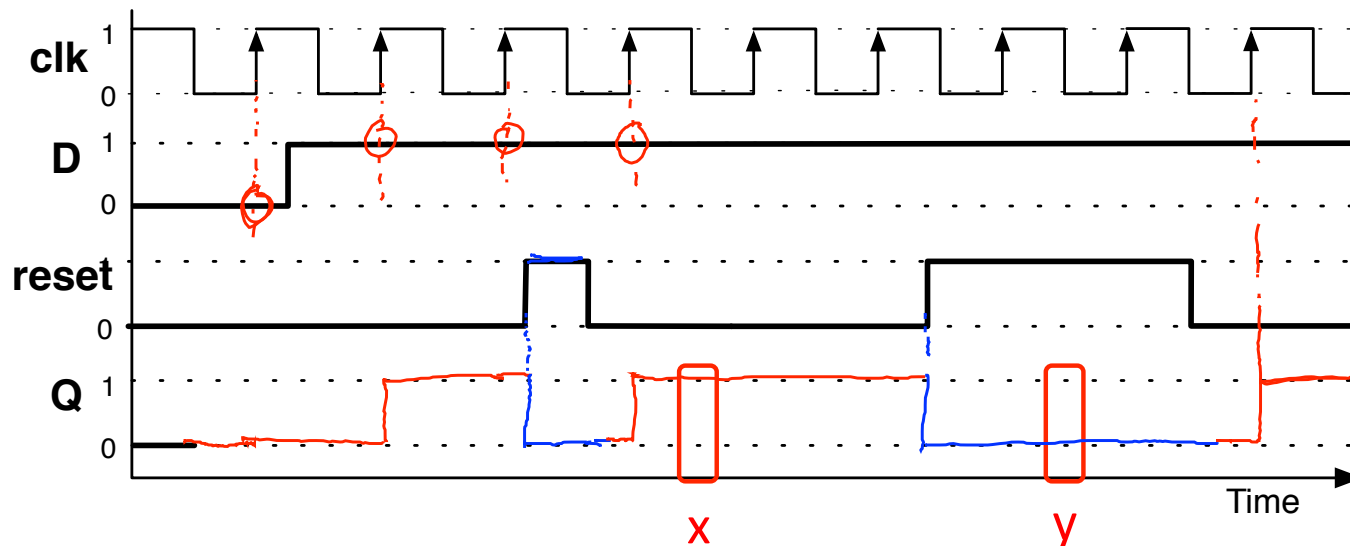 
# Asynchronous reset immediately resets a flip-flop to 0


- **Asynchronous** = pertaining to operation without the use of fixed time intervals (opposed to synchronous).



x,y =  
a) 0,0  
b) 0,1  
c) 1,0  
d) 1,1

# Asynchronous Reset implementation



One example possible implementation

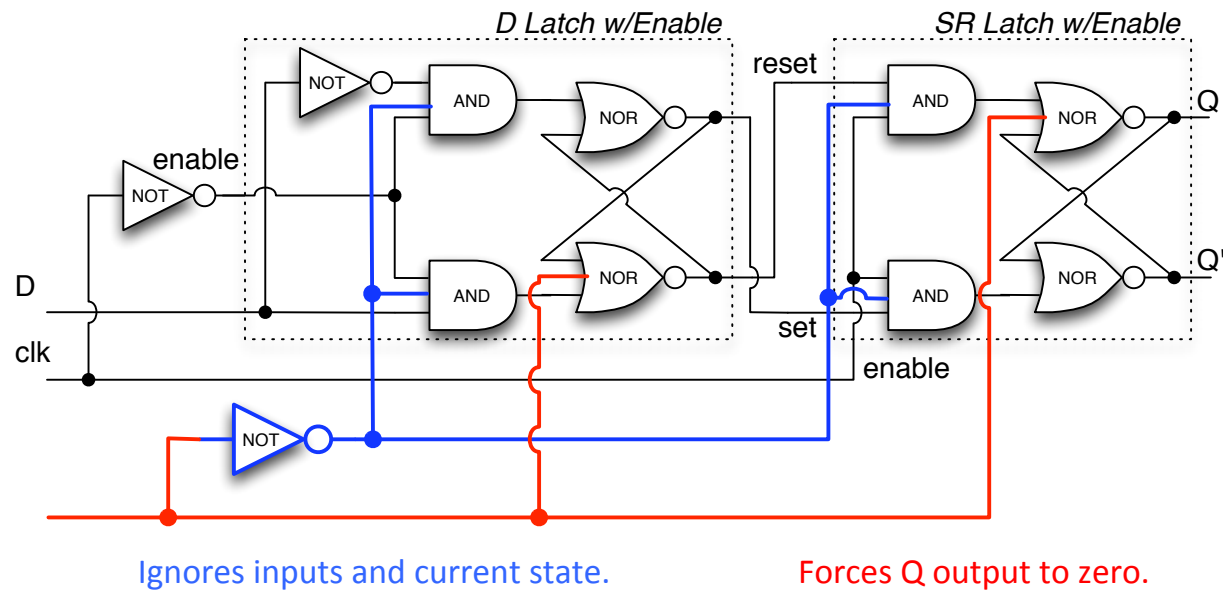

(Not required material)

# When enable is 0, the flip flop doesn't change on the rising edge

- Behaves normally when enable=1

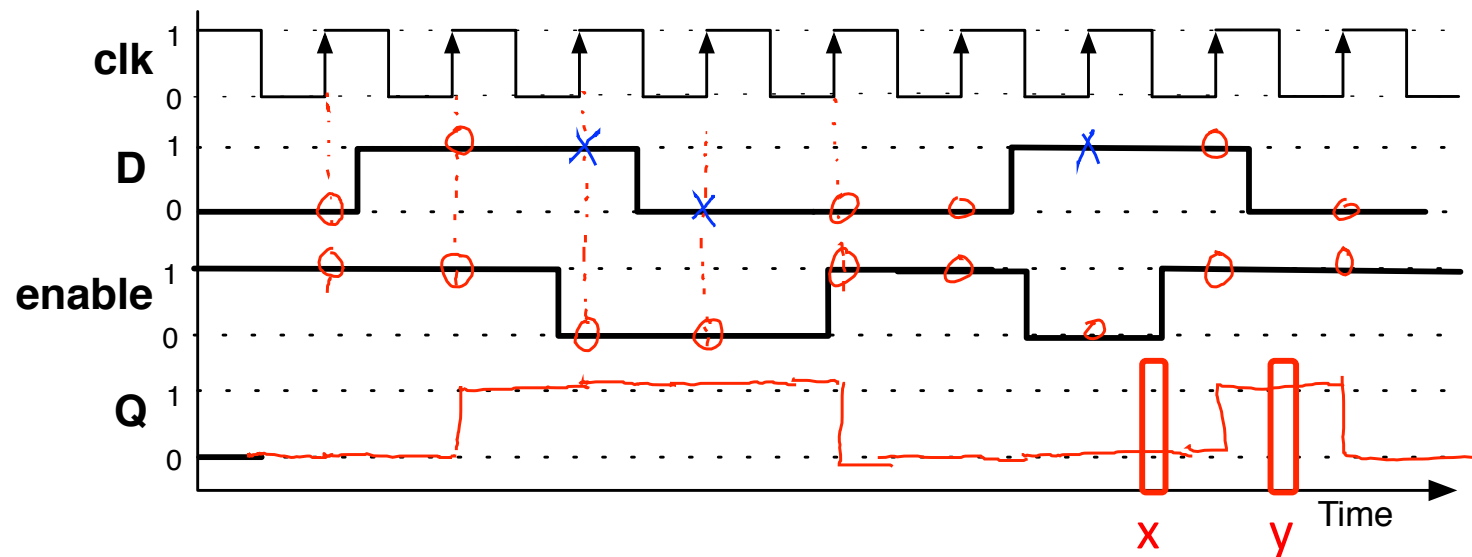 

x,y =  
a) 0,0  
b) 0,1  
c) 1,0  
d) 1,1

$$2^2 = 4$$

2  
Address bits × 8  
Data bits



00



01



10



11



3 × 8  
Address bits × Data bits





4 × 8  
Address bits × Data bits



2 × 8  
Address bits × Data bits



00



01



10



11



2 × 16  
Address bits × Data bits



00



01




10



11




2 × 32  
Address bits × Data bits

 

# Use multiple **flip flops** to build **registers**

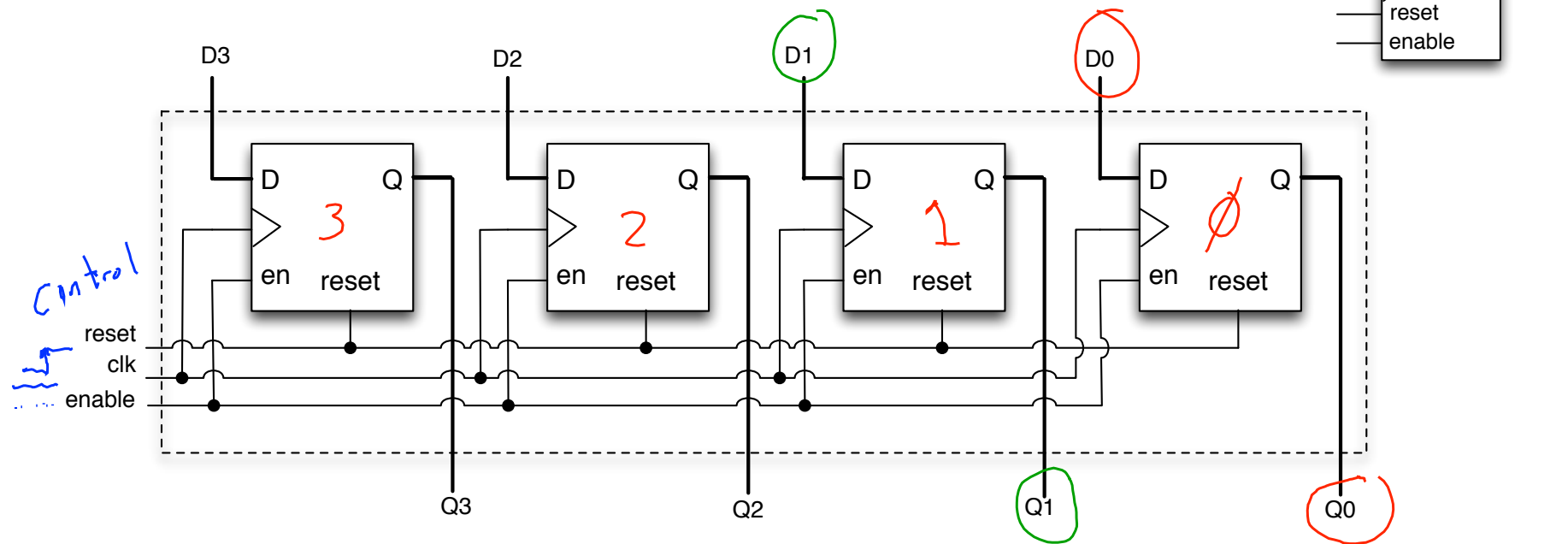- Example **4-bit register** made of **four D flip flops**
  - All **control** signals use the same input



# Random Access Memory (RAM) is the hardware equivalent of an array

Addr

- RAM stores **data** at **addresses**
- All **data** has the same bit width
- Use brackets to access **data** at any **address**

M[Addr]

idx

- Arrays store **data** at **indices**
- All **data** has the same type
- Use brackets to access **data** at any **index**

**Array**[idx]

# RAM is the hardware equivalent of an array

- The **address** is an array index.
  - A  $k$ -bit **address** can specify one of  $2^k$  words
- Each **address** refers to one word of data.
  - Each word can store  $N$  bits

$2^k \times N$  memory  
↑      ↑  
# loc   # bits / loc

Address	Data
00000000	
00000001	
00000002	
.	
.	
.	
.	
.	
.	
.	
.	
.	
.	
FFFFFFFD	
FFFFFFFE	
FFFFFFF	

## A RAM should be able to

1. Store many words, one per address
2. Read the word that was saved at a particular address ( $??? = \underline{M}[\underline{Addr}]$ )
3. Change the word that's saved at a particular address ( $\underline{M}[\underline{Addr}] = \textcircled{???}$ )




# A Register File is a synchronous RAM

Use the letter R to indicate that the RAM is a register file rather than a generic memory (M)

$R[7]$


$R[Addr]$

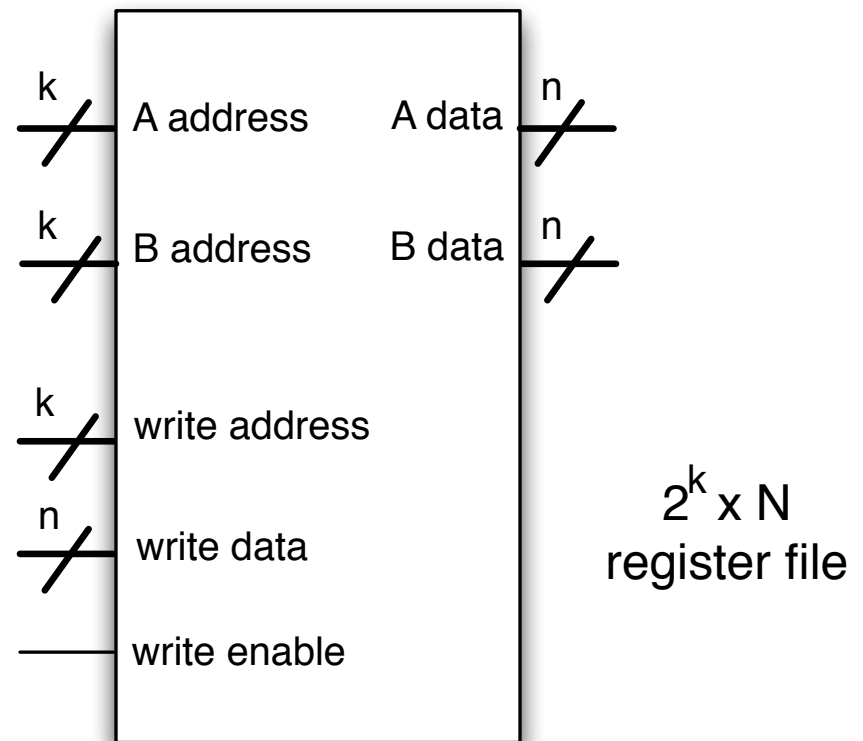
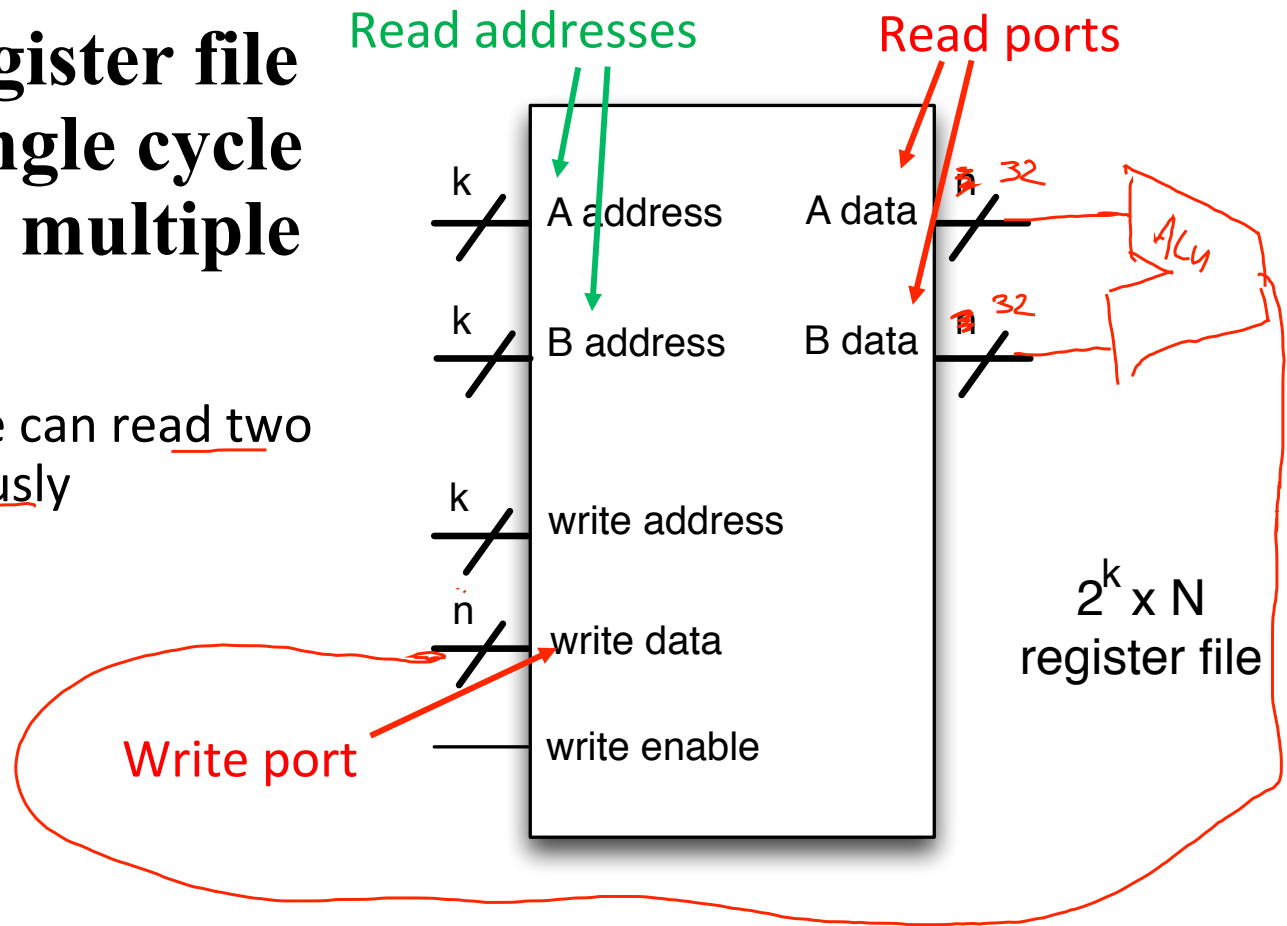
# Our MIPS register file will enable single cycle operations on multiple data

- 2 read ports, so we can read two values simultaneously
- 1 write port

$n = 32b$   
 $32 \text{ regs}$   
 $2^k = 32$



## clicker question

$2^7$   
↓

We need to build a RAM that can store 128, 64-bit words and has one write port and three read ports

How many address bits does my RAM need for its write port?

- A) 1
- B) 6
- C) 7
- D) 64
- E) 128

## clicker question

We need to build a RAM that can store 128, 64-bit words and has one write port and three read ports

How many data bits does my RAM need for each read port?


- A) 3
- B) 6
- C) 7
- D) 64
- E) 128

# Let's build a 2-word memory with 4-bit words

$$2^1 = 2$$


A register file has 3 parts

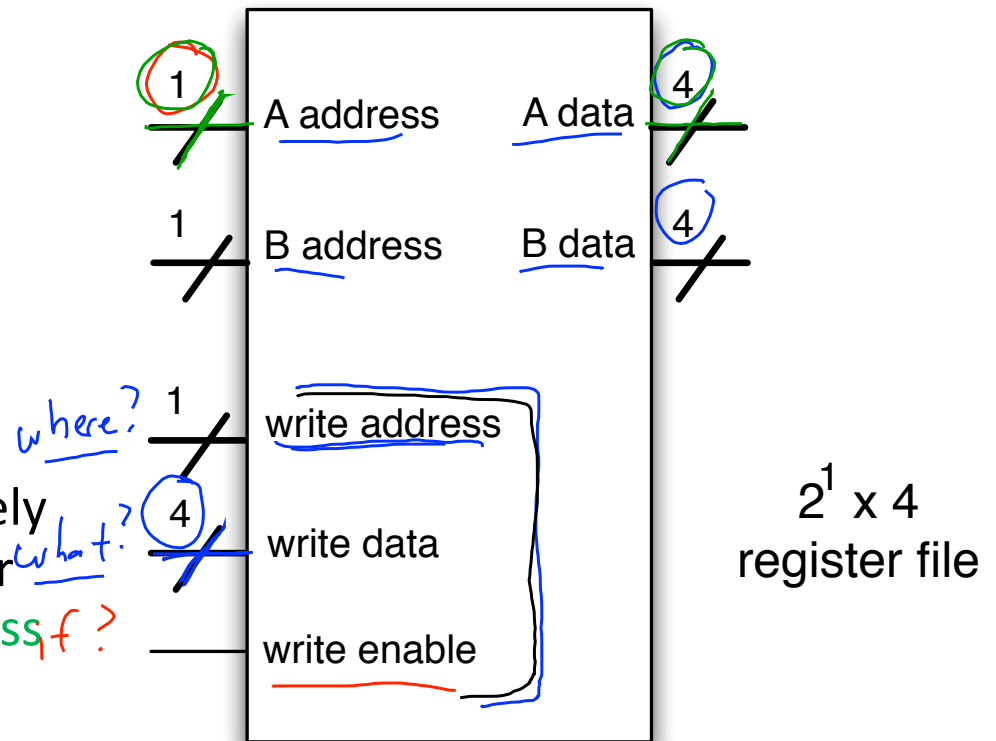1. **The Storage**: An array of registers
2. **The Read Ports**: Output the **data** of the register indicated by read **addresses**
3. **The Write Port**: Selectively write **data** to the register indicated by write **address** **what?**



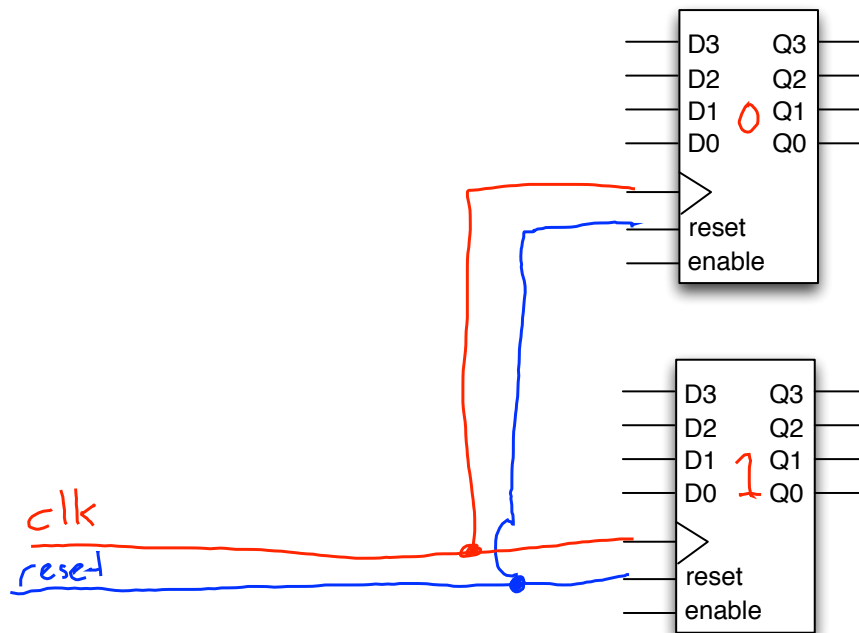
## Step 1: Allocate 1 register per address ( $2^1 \times 4$ ) <sup>5-46</sup>

- Wire clocks and resets together to maintain synchronization




Step 2: Read ports use the address to select one register's **data** to output

A address

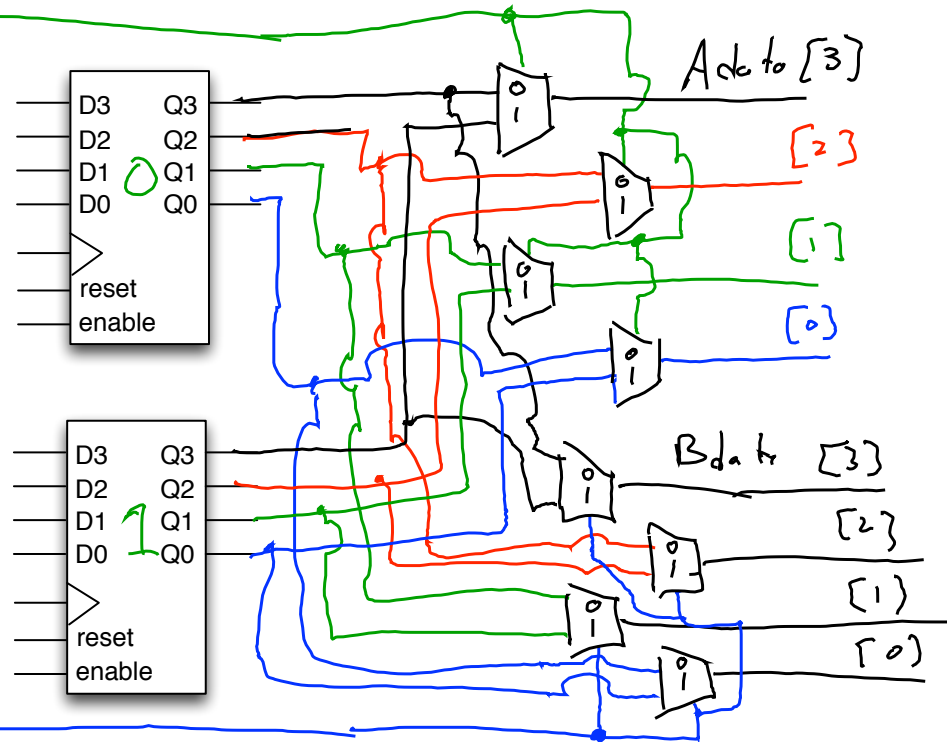

B Address

 
**Step 3: Write ports decode the address to enable writing to exactly one register**




 
## Decoders receive a binary code to generate **control** signals


- A **1-to-2** Binary decoder receives a 1-bit unsigned binary code and an enable signal to enable one of two devices




EN	$A_0$	$(E_1, E_0)$
0	X	(0, 0)
1	0	(0, 1)
1	1	(1, 0)

Handwritten green annotations: Under the  $A_0$  column, '0' and '1' are underlined. In the row (1, 0), the '1' is circled. Below the table, the numbers 2, 1, 0 are written, with a '1' written below the '1' in the third row.

 n-to-2<sup>n</sup> Binary decoders receive n-bit unsigned binary codes to enable one of 2<sup>n</sup> devices




EN	A[1:0]	E[3:0]
0	X	(0,0,0,0)
1	(0,0)	(0,0,0,1)
1	(0,1)	(0,0,1,0)
1	(1,0)	(0,1,0,0)
1	(1,1)	(1,0,0,0)


 


EN	A[4:0]	E[31:0]
0	X	0x0000
1	0	0x0001
1	1	0x0002
...	...	...
1	30	0x4000
1	31	0x8000
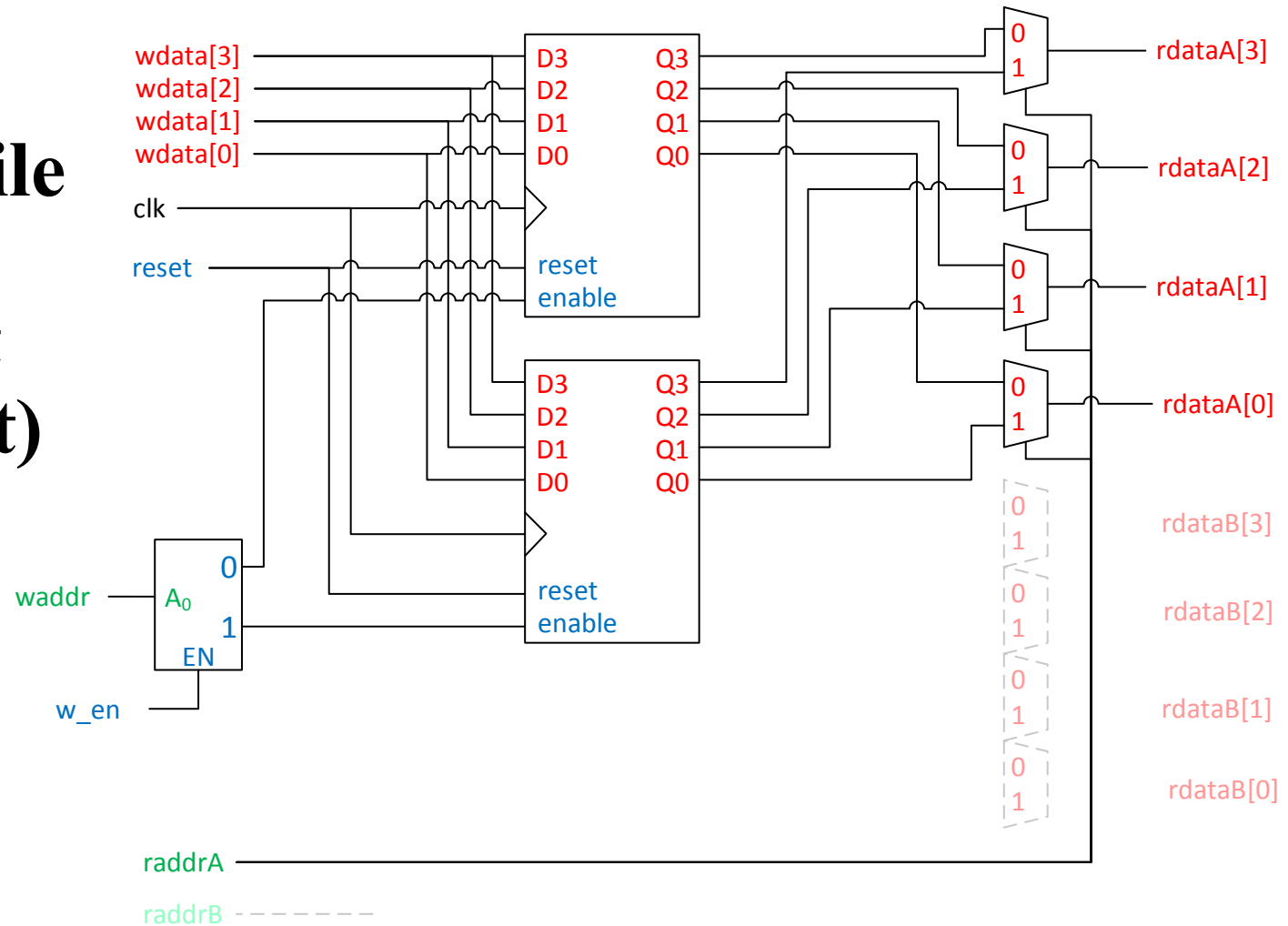
# 2<sup>1</sup> x 4-bit register file (only 1 read port fully built)






# What does it do?

 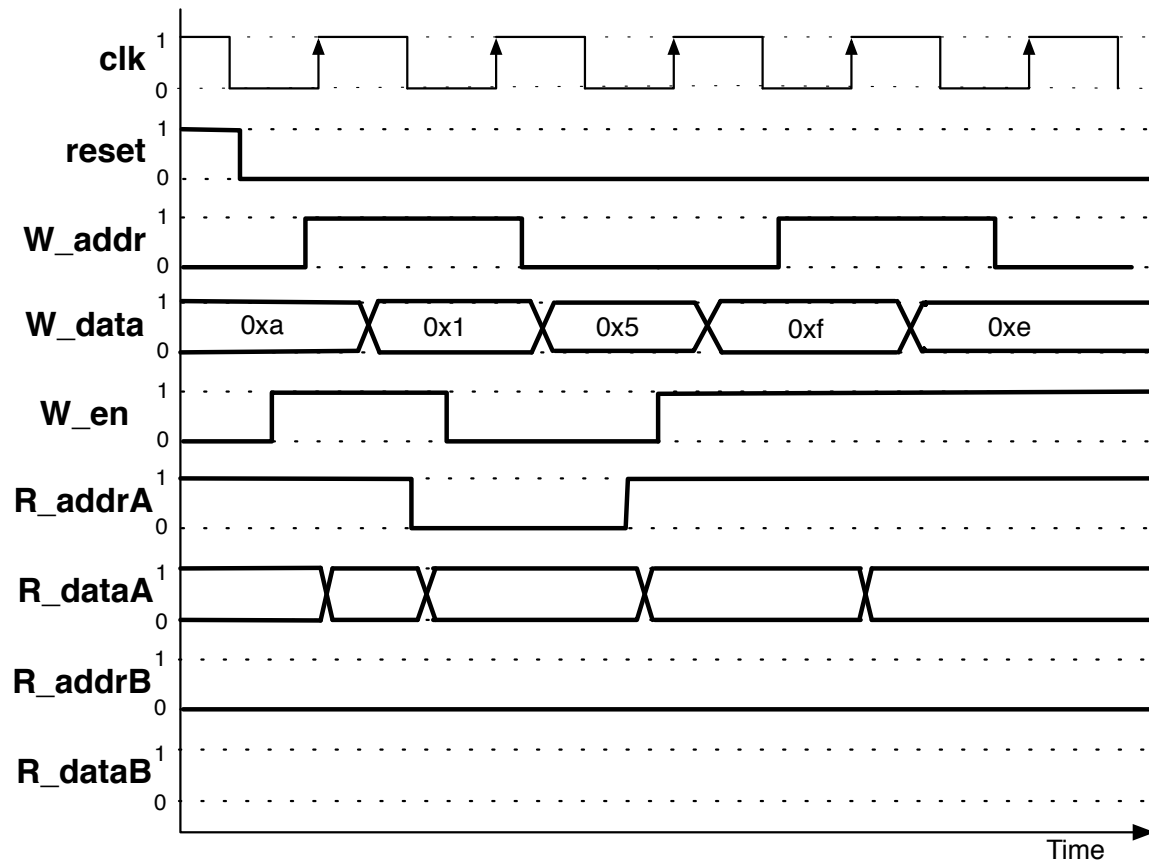

- a) 0x0
- b) 0xa
- c) 0x1
- d) 0x5
- e) 0xf

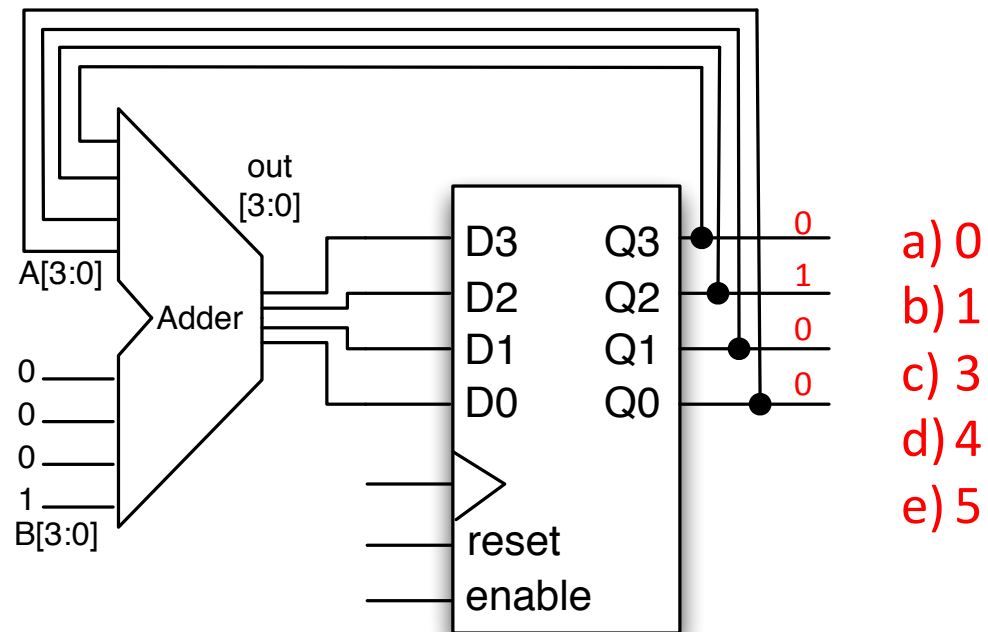**What will Q[3:0] be during the next clock cycle?**



 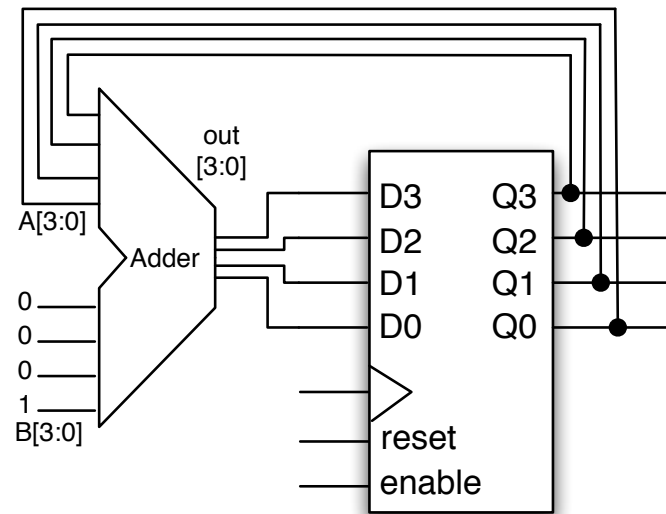

- a) 0x0
- b) 0x2
- c) 0x4
- d) 0x6
- e) 0x8

# Implementing counters

