


Designing a calculator FSM

<https://www.theonlinecalculator.com/>

Design the FSM for parsing an input string for a calculator


What must the finite state machine remember to execute the operation

$1+2?$

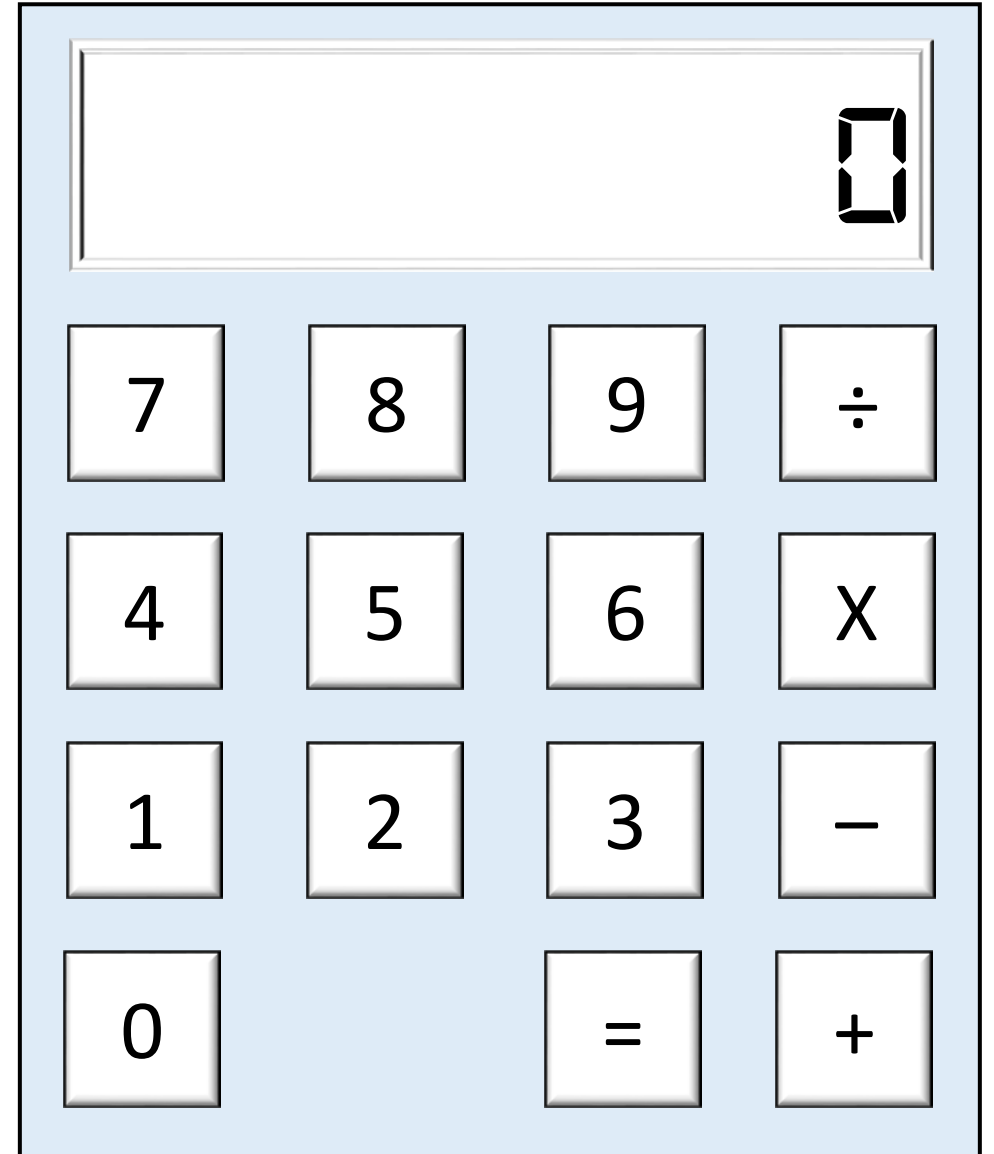


**Try one on your own:
Draw a state diagram for**


$$2+2+5$$

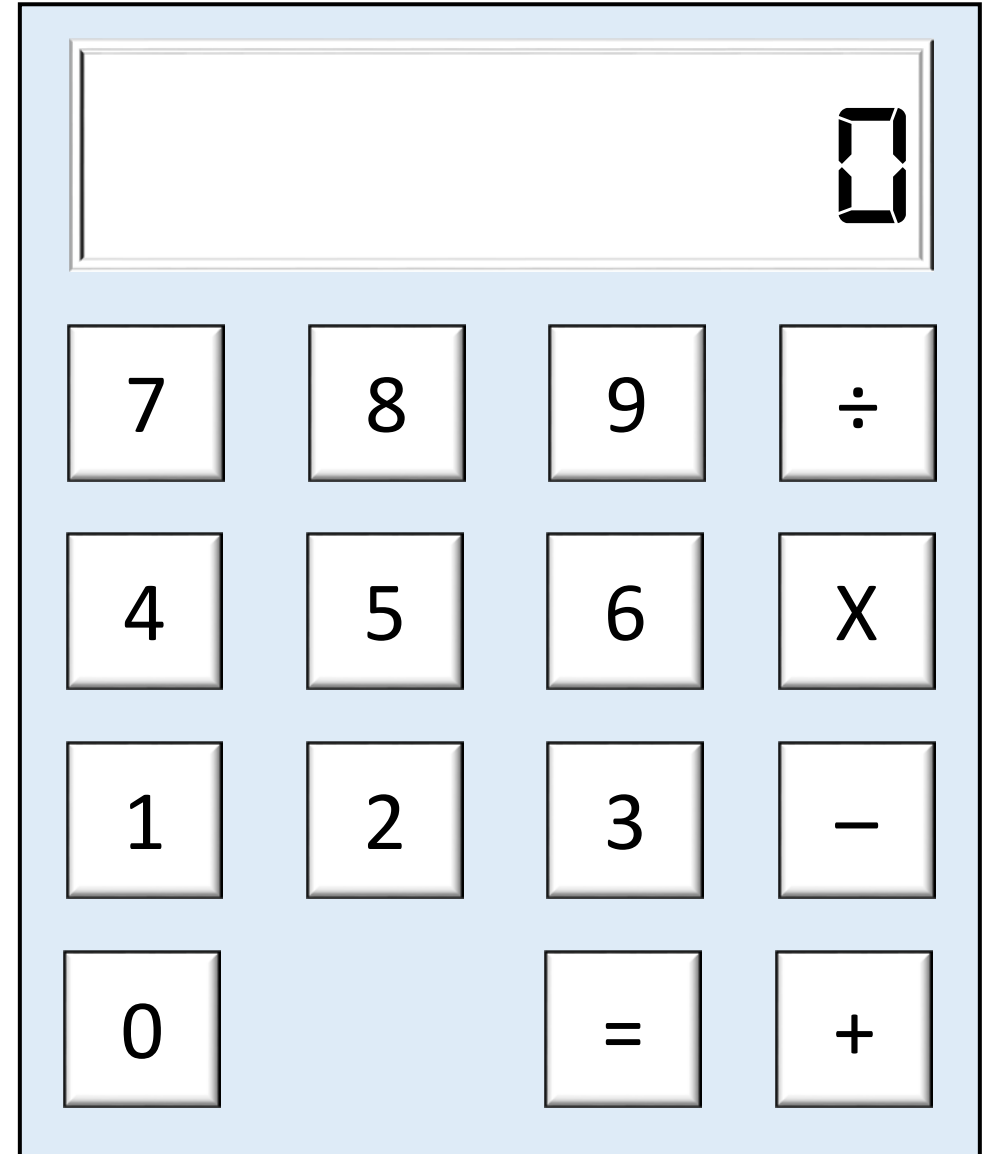

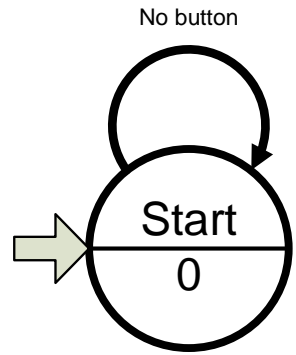Let's build a FSM that allows for several operations and data sequences



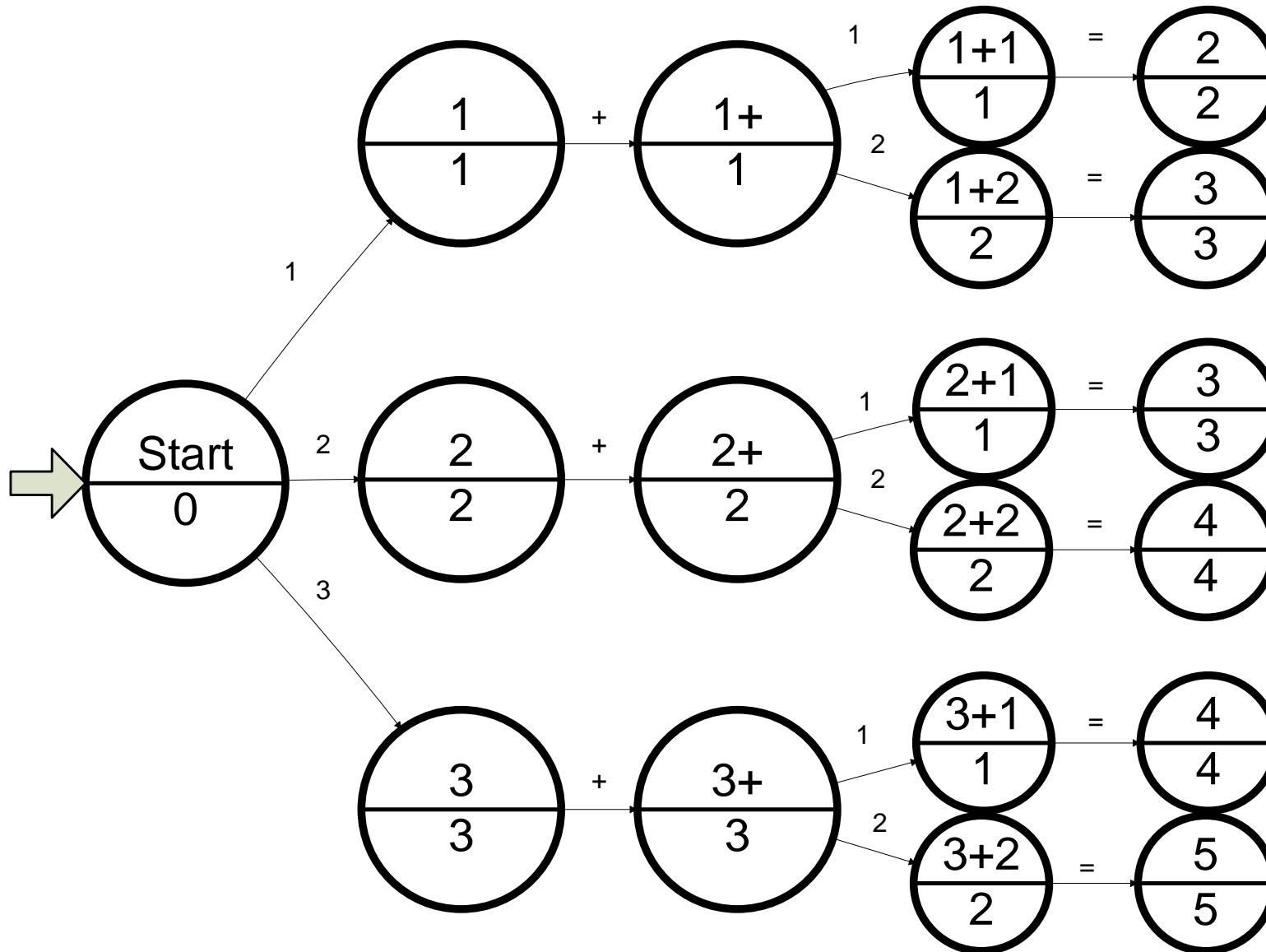
Separate the **data** from the **control** using **indirection** (self loops are implicit to minimize clutter)



operand1, operand2,
operator, and result
are data

Start state and
“which data has been
entered” are control

Offload **data** onto external variables

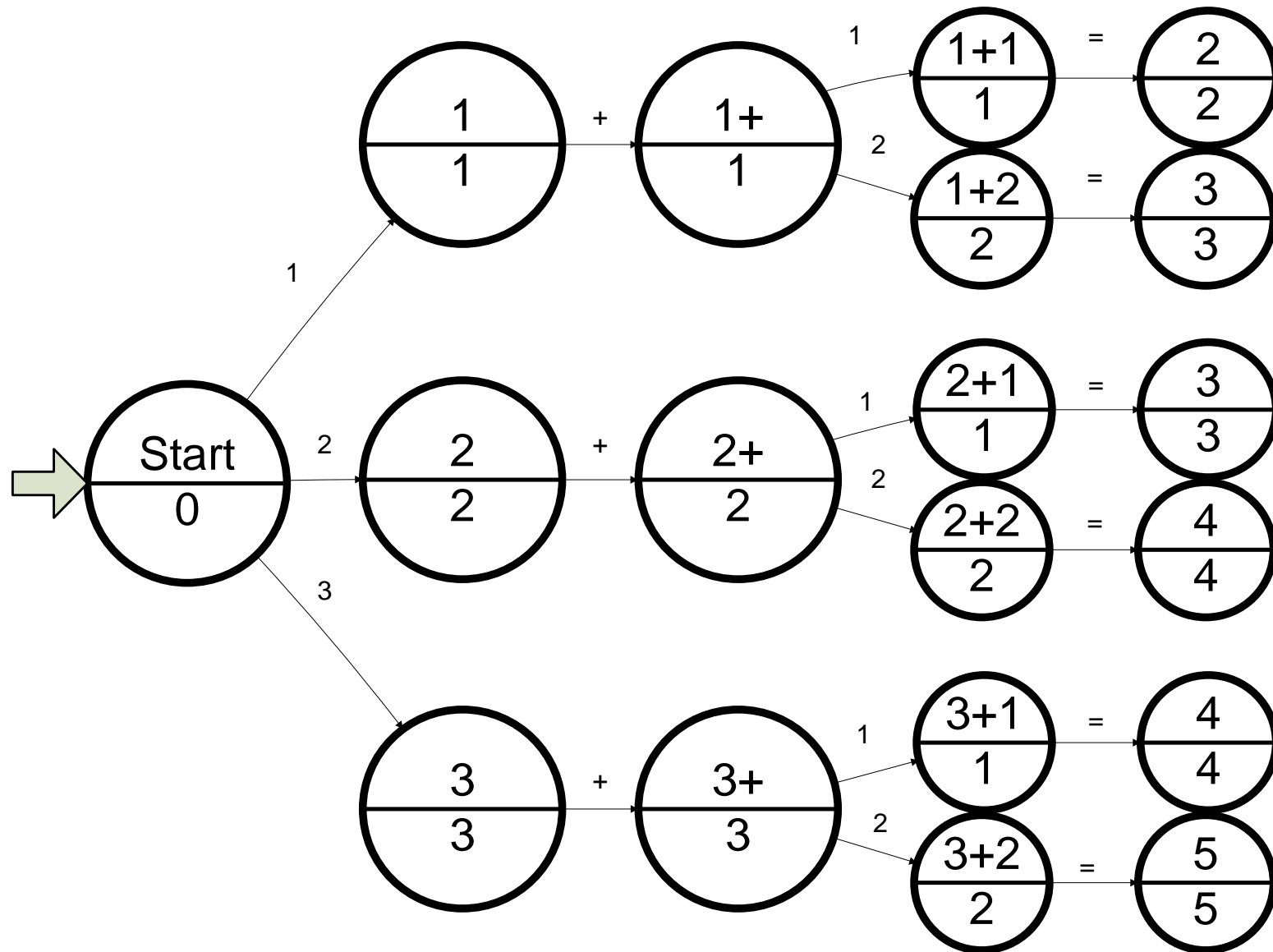


operand1 (op1)

operand2 (op2)

operator (op)

result (res)

Our generalized calculator FSM so far

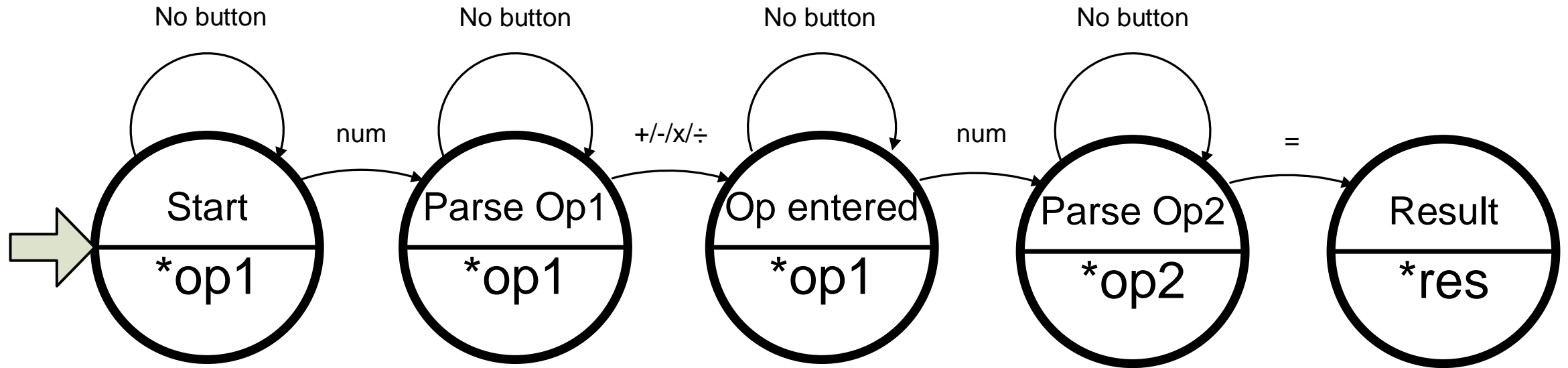

What else do we still need
this state machine to do?


operand1 (op1)

operand2 (op2)

operator (op)

result (res)

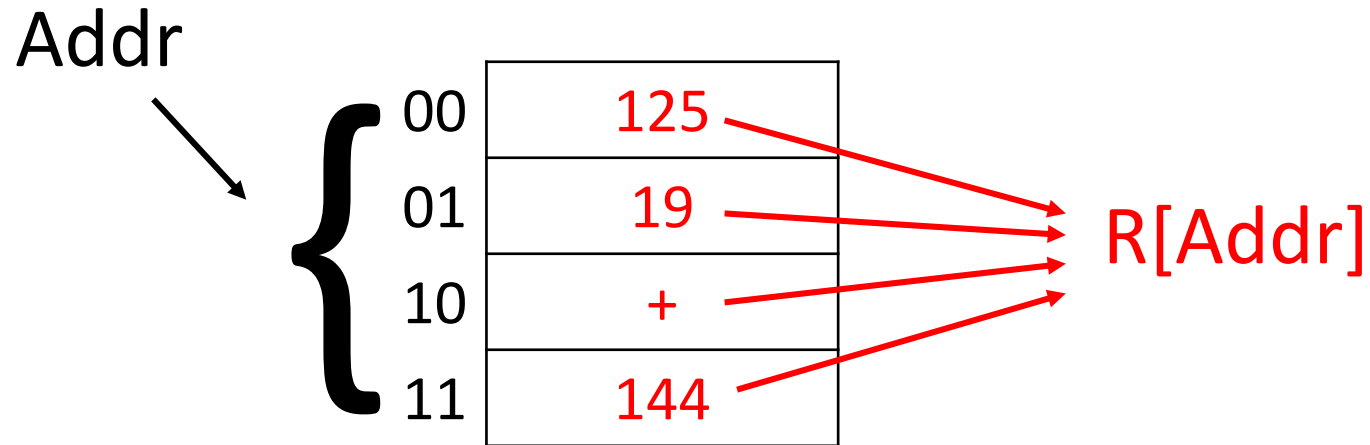Use brackets to indicate the data stored at an address in an array (a.k.a. a register file)



Use the FSM and system input to **control** the register file and ALU (the **datapath**)

Keypad

DISPLAY

In

Keypad input Current State
Calculator Control FSM
Display Output

WAddr
WData

EN $2^2 \times 27$ Reg File
BAddr BData
AAddr AData
DAddr DData

B
A
ALU